

# **Data Conversion and Lab (17.368)**

**Spring 2013**

## **Lecture Outline**

Class # 04

September 26, 2013

Dohn Bowden

# Today's Lecture Outline

- Administrative
- Detailed Technical Discussions
  - Analog to Digital Conversion
- Lab
  - Finish Lab #2
  - Start Lab #3 (obtain parts and wire board for next week)
- Homework

# Course Admin

# Syllabus Review

<i>Week</i>	<i>Date</i>	<i>Topics</i>	<i>Lab</i>	<i>Lab Report Due</i>
<del>1</del>	<del>09/05/13</del>	<del>Introduction/Basic Data Conversion, Course Overview, Op Amps in Data Conversion</del>		
<del>2</del>	<del>09/12/13</del>	<del>Op Amp Lab</del>	<del>1</del>	
<del>3</del>	<del>09/19/13</del>	<del>Sample and Hold Lecture and Lab</del>	<del>2</del>	
4	09/26/13	A/D Conversion Fundamentals and Lab	3	1
5	10/03/13	A/D Conversion Lab Continuation	3 con't	
6	10/10/13	<b>Examination 1</b>		
7	10/17/13	D/A Conversion Fundamentals and Lab	4	2
8	10/24/13	D/A Conversion Lab Continuation		
9	10/31/13	Microcontroller and Sensors	4 con't	3
10	11/07/13	Microcontroller and Sensor Lab	5	
11	11/14/13	V/F and F/V Conversion Lecture	5 con't	4
12	11/21/13	<b>Examination 2</b>	Project	5
<b>X</b>	<b>11/28/13</b>	<b>No Class – Thanksgiving</b>		
13	12/05/13	Work on Course Project	Project	
14	12/12/13	Final Exam/Course Project Brief and Demonstration	Demo	

# Class Hours

- Thursdays evenings ... 6:30 – 9:20 PM ...
  - **Lectures in BL-407????**
  - Labs will be in BL-407 ... (AFTER THE LECTURE)????

# **Detailed Technical Discussion**

# References ...

# References

- Lecture material is covered in the text as follows ...
  - Data Conversion Handbook
    - On line version (PDF)
      - Section 3.2, pages 3.39 – 3.103
      - Section 3.3, pages 3.109 – 3.133
    - Textbook (Hard Copy)
      - Pages 175 – 224
      - Pages 231 – 248
- Continued next page ...




## References ... continued

- “Understanding analog to digital converter specifications”, by Len Stellar. Embedded Systems Design, 02/24/05
- Which ADC Architecture is Right for Your Application, by Walt Kester. Analog Dialogue 39-06, June 2005
- Freescale Semiconductor Application Note AN2438/D 2/2003


**The above articles can be found on the class web page**

# ADC Overview ...

# Analog To Digital Conversion Overview

 

# Basic ADC with External References

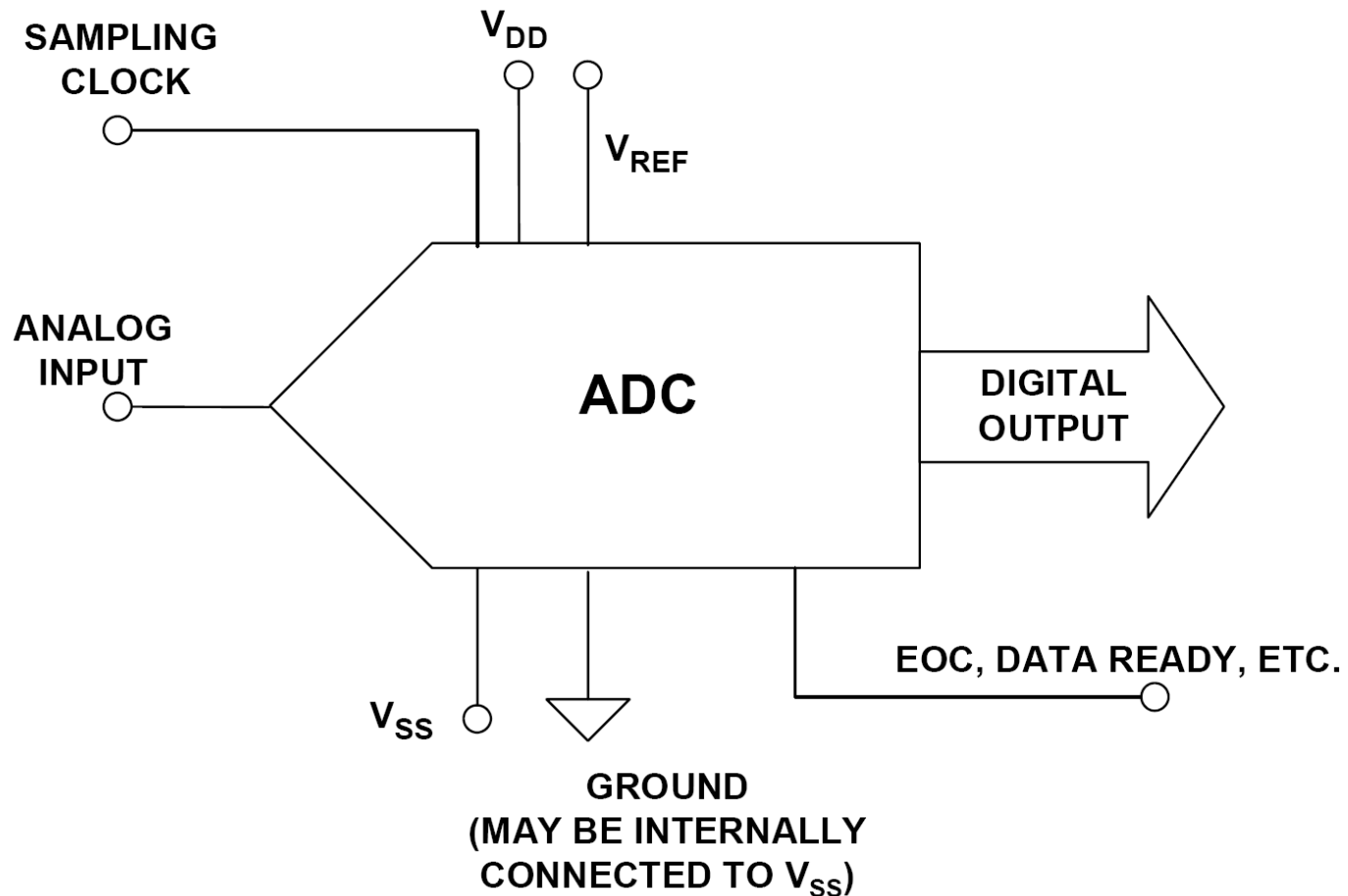

# Analog To Digital Conversion Overview

- Analog to Digital conversion is a straight forward process
- We will be looking at the steps involved in the conversion
- We will look at the various architectures for ADCs

# Sample and Hold ...

# Sample and Hold

- Use to be separate IC
  - Today ... most ADC include Sample and Hold circuitry
- Just because we don't see a separate Sample and Hold circuit ... does not mean we can ignore it!
- Recall ... the Sample and Hold circuit will hold the analog value constant during the Analog to Digital conversion process
  - If the analog signal changes half way through the process
    - Our conversion will be corrupt!

# Sampling ...



# Sampling

- *Sampling* is ...
  - The reduction of a continuous signal to a discrete signal
  - Specifically ... *Sampling* is the process of analyzing the continuous analog signal with measurements taken at discrete and standard intervals
    - An example ... the conversion of a sound wave (a continuous-time signal) to a sequence of samples (a discrete-time signal)

# How Often Do We Sample the Signal?

- We sample based on the *Nyquist* Criteria ... which is ...
  - A signal with a maximum frequency  $f_a$  must be sampled at a rate ...

$$f_s > 2f_a$$

- ... Or information about the signal will be lost because of *aliasing*
  - » Where  $f_s$  is ... the sampling frequency
  - » And  $f_a$  is ... the maximum signal frequency


## Simply Stated ...

- The *Nyquist* criteria requires that the sampling frequency be ...
  - ... at least twice the highest frequency contained in the signal or information about the signal will be lost
- If the sampling frequency is less than twice the maximum analog signal frequency ...
  - a phenomena known as *aliasing* will occur


# *Aliasing*

- *Aliasing* is the result of not sampling the analog signal at a high enough rate
- This will produce low-frequency signals (also called *aliases*) that cannot be distinguished from the signal


# Sampling at $f$

 


## Sampling at $2f$

 

# Sampling at $4f/3$

 

# Sampling at many times per cycle

 



## Therefore ...

- As the sampling rate increases ...
  - The more signal values we gather to represent the analog signal
  - And you would think the more accurately you would represent the signal!
    - This is not true!
- It has been proven mathematically ...
  - That in order to reconstruct an analog signal from its sample points ...
    - All we need is to sample at a rate at least twice as fast as the highest frequency component of the signal
- This minimum sampling frequency ... known as the *Nyquist Rate*

# In Practice Sampling Rate ...

- In practice ... as a rule of thumb ...
  - We like to sample the analog signal at a rate ...  
5 to 10 times the highest frequency component

# Quantization ...

# Quantization

- *Quantization* is ...
  - The procedure of constraining something from a continuous set of values (such as the real numbers) ...
  - ... to a discrete set (such as the integers)

# Quantization


- The ADC represents an analog signal as a digital string of 1's and 0's with finite resolution
  - The ADC outputs a finite number of digital values ...
    - equal to  $2^N$   
(where N is the number of bits of the ADC)

# Amplitude Quantization ...

# Amplitude Quantization

- *Amplitude Quantization:*
  - The maximum amplitude range of an analog signal must be divided into a fixed number of small, equal intervals
  - Each interval is then associated with a fixed binary number
    - The A/D Converter performs such a function
  - Factors that must be specific for an A/D Converter:
    - The maximum range of analog input voltage (Full Scale)
    - The output resolution (determined by the number of output bits)

# Amplitude Quantization

 



**Full Scale ...**

# Full Scale

- *Full Scale* (FS) ...
  - The input range (span) of analog voltage accepted by the converter
    - (i.e. 0 to 10 volts)
- In converter technology ... *Full Scale* (FS) is independent of the number of bits of resolutions (N)
  - We will discuss bits of *resolution* (N) later

# Resolution ...

# Resolution

- **Resolution** ... Is a measure of the smallest change in analog input that can be discriminated by an A/D Converter
  - The more binary digits of output that are available ...
  - The more resolution that is possible, and ...
  - The more precision we can encode the analog signal
- The **resolution** of an '**N**' bit A/D converter with a voltage range of "**0 – X**" volts is ...

$$\frac{X - 0}{2^N} \quad \text{or} \quad V_{step} = \frac{V_{max} - V_{min}}{2^N}$$

# Example

- For a 4 bit converter
- Zero to fifteen volts input range
- We have

$$\text{volt} \quad \frac{X - 0}{2^N} = \frac{15}{2^4} = \frac{15}{16} = 0.9375 \text{ per}$$

- The output of an A/D Converter is said to be accurate to within  $\pm \frac{1}{2}$  LSB (Least Significant Bit)
- Hence, the accuracy of the above example would approximately be  $\pm 0.47 \text{ V}$

## Example

- For an 12-bit A/D Converter with a voltage range of 0 – 10 Volts, what would the resolution be?

$$\frac{10}{(2^{12})} = \left( \frac{10}{4096} \right) = 2.44mV$$

# Example

- Assume a voltage range of 0 – 10 Volts with a 14-bit A/D Converter ... what would the resolution be?

$$\frac{10}{(2^{14})} = \left( \frac{10}{16,384} \right) = 0.61mV$$

- At this level of resolution, unavoidable noise of equal or greater amplitude generated within the analog circuitry of the A/D Converter would cause errors and signal information to be lost and not recoverable

## Example

- For an 14-bit A/D Converter with FS voltage range (-10 to +10 Volts)

What is the resolution?

$$\frac{10 - (-10)}{(2^{14})} = \left( \frac{20}{16384} \right) = 1.22mV$$




# **ADC Specifications ...**

# ADC Specifications

- ADCs convert an analog signal input to a digital output code
- ADC measurements deviate from the ideal due to ...
  - Variations in the manufacturing process ... and ...
  - Through various sources of inaccuracy in the analog-to-digital conversion process
- The ADC performance specifications will quantify the errors that are caused by the ADC itself

# Ideal transfer function of a 3-bit ADC

 

# ADC Specifications

- ADC performance specifications are generally categorized in two ways ...
  - DC accuracy ... and ...
  - Dynamic performance

# DC Accuracy

- Offset error
- Full-scale error
- Differential Nonlinearity (DNL)
- Integral Nonlinearity (INL)

# Dynamic Performance

- Signal-to-noise ratio (SNR)
- Harmonic distortion
- Signal-to-noise and distortion (SiNAD)
- Spurious-free dynamic range

# ADC Specifications

- For an in-depth look at ADC specifications ...
  - Read ...
    - “Understanding analog to digital converter specifications”  
by Len Stellar  
Embedded Systems Design, 02/24/05  
Link is on the course web site ...

# **ADC Architectures ...**




# Analog to Digital Converter Architectures

- Most ADC applications today can be classified into four broad market segments:
  - Data acquisition
  - Precision industrial measurement
  - Voiceband and audio
  - “High speed”
    - Implying sampling rates greater than about 5 MSPS

# Analog to Digital Converter Architectures

- A very large percentage of the previously stated applications can be filled by
  - Successive-approximation (SAR)
  - Sigma-delta ( $\Sigma$ - $\Delta$ )
  - Pipelined ADCs
 
# ADC Architectures, Applications, Resolution, and Sampling Rates



# Types of ADCs

- ADCs can be grouped into many different categories ...
  - Architecture type
  - Speed
  - Resolution
  - Power consumption

... to mention just a few

# Successive Approximation Register (SAR) ADC...


# Successive-Approximation-Register or SAR ADC

- A **successive-approximation-register** or SAR ADC ...
  - Is more complex than some of the other ADC architectures
- But there are advantages to the complexity
  - The SAR ADC works by using a single comparator to compare the input analog voltage to an internal reference voltage for each bit in the conversion
    - Therefore ... the input signal needs to be compared ten times for an 10-bit resolution converter

## Successive-Approximation-Register (con't)


- As each comparison takes place ...
  - a binary value of the approximation is stored in a register
- As comparisons and approximations continues ...
  - The register shifts to the next most significant bit until the word is complete
- This architecture is not the fastest ... but ...
  - It can provide an accurate approximation of the analog signal

# Successive Approximation ADC Algorithm

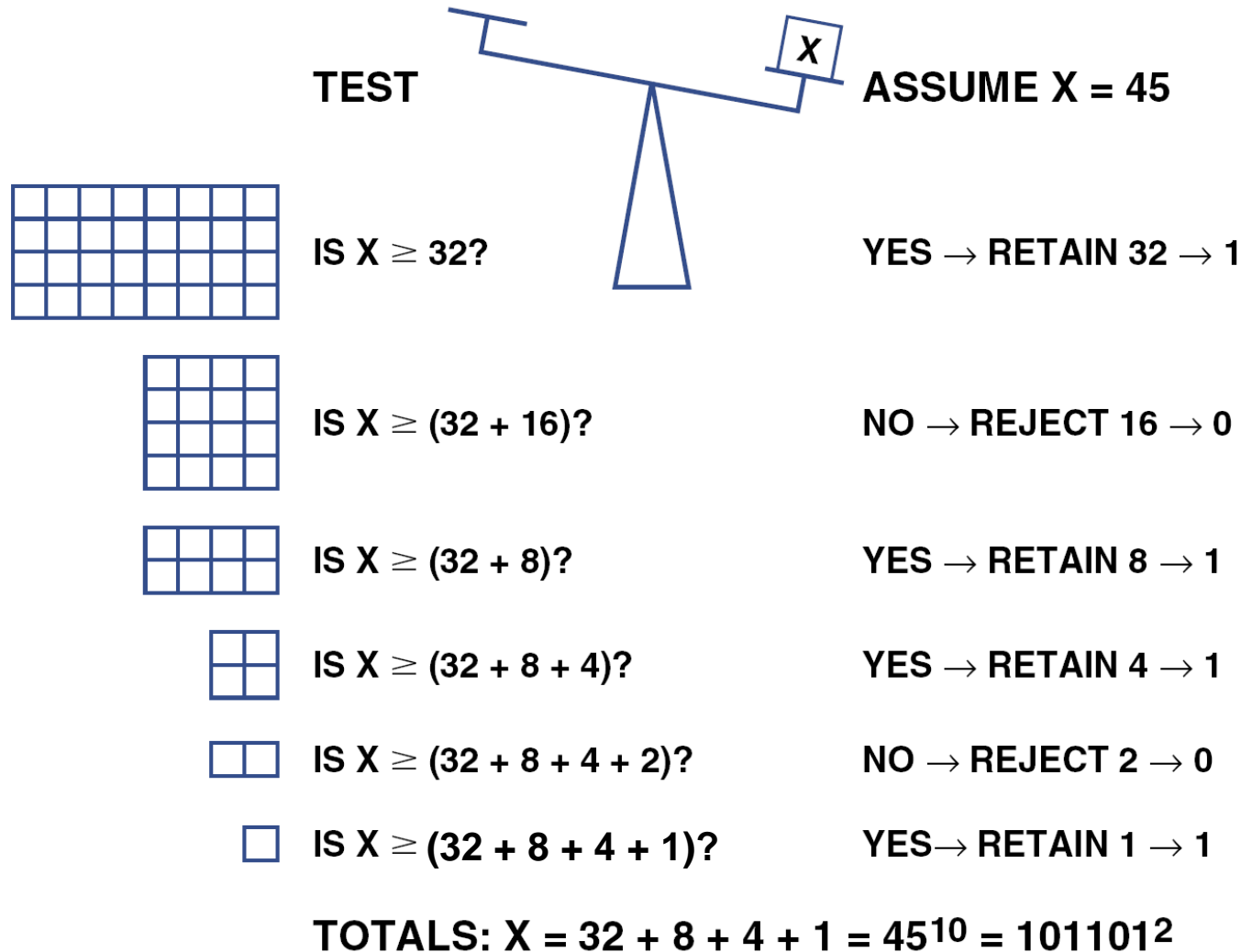



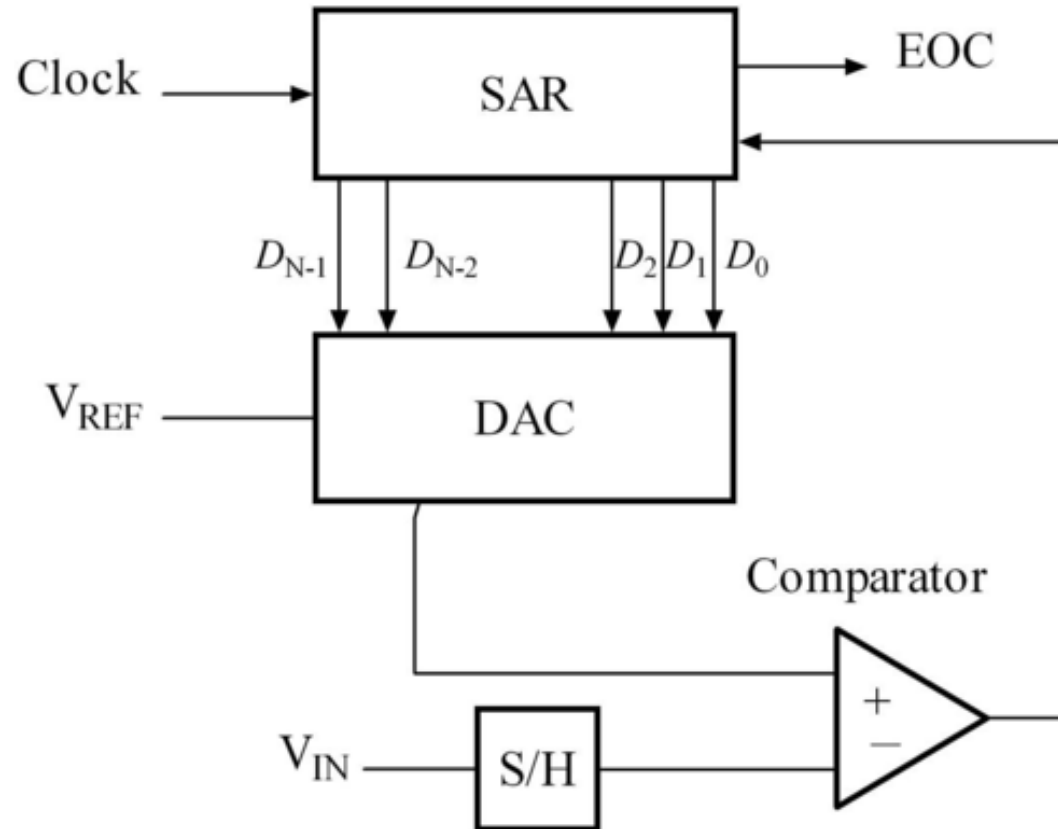
# Successive Approximation ADC Block Diagram


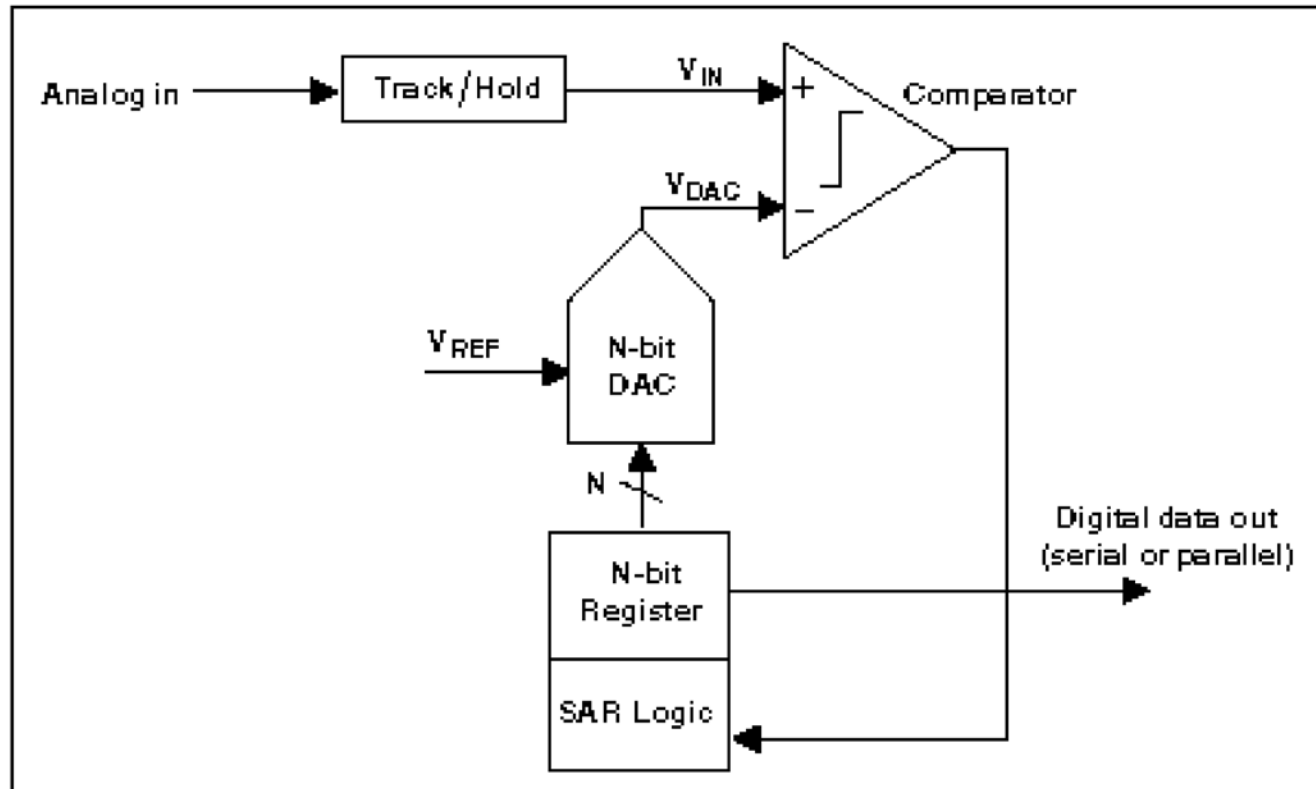
## *Simplified N-bit SAR ADC architecture*



# Successive-Approximation-Register (SAR) ADC

- The SAR ADC circuit typically consists of four components:
  - A sample and hold circuit
  - An analog voltage comparator
    - Compares  $V_{in}$  to the output of the internal DAC
    - Results of the comparison goes to the register
  - A successive approximation register
    - Supplies an approximate digital code of  $V_{in}$  to the internal DAC
  - An internal reference DAC
    - Supplies the comparator with an analog voltage equivalent of the digital code output of the SAR for comparison with  $V_{in}$


# Successive Approximation ADC Algorithm

- The SAR is initialized so that the most significant bit (MSB) is equal to a digital 1
- The DAC supplies the analog equivalent of this digital code ( $V_{ref}/2$ ) into the comparator circuit for comparison with the sampled input voltage
- If this analog voltage exceeds  $V_{in}$  the comparator causes the SAR to reset this bit and set the next bit to a digital 1
- If it is lower then the bit is left a 1 and the next bit is set to 1

## Successive Approximation ADC Algorithm (con't)

- This search continues until every bit in the SAR has been tested
- The result is the digital approximation of the sampled input voltage and ...
  - The digital value is provided by the ADC at the end of the conversion

## Example --- 4-bit conversion

 

- The first comparison shows that  $V_{IN} < V_{DAC}$ 
  - Bit 3 is set to '0'
  - The DAC is then set to 01002
- The second comparison is performed
  - $V_{IN} > V_{DAC}$  so bit 2 remains at '1'
  - The DAC is then set to 01102
- The third comparison is performed
  - Bit 1 is set to '0'
  - The DAC is then set to 01012 for the final comparison
- Finally, bit 0 remains at '1' because  $V_{IN} > V_{DAC}$


# **Sigma-Delta ( $\Sigma$ - $\Delta$ ) ...**

# Sigma-Delta ADC

- **Sigma-Delta** (AKA ... Delta-Sigma) converters have relatively simple structures
  - a modulator
  - a digital decimation filter
- The modulator has ...
  - an integrator ... and ...
  - a comparator with a feedback loop that contains a 1-bit digital-to-analog converter
- The sigma-delta ADC also includes a clock that provides timing for the modulator and digital decimation filter



# First-order Sigma-Delta ADC

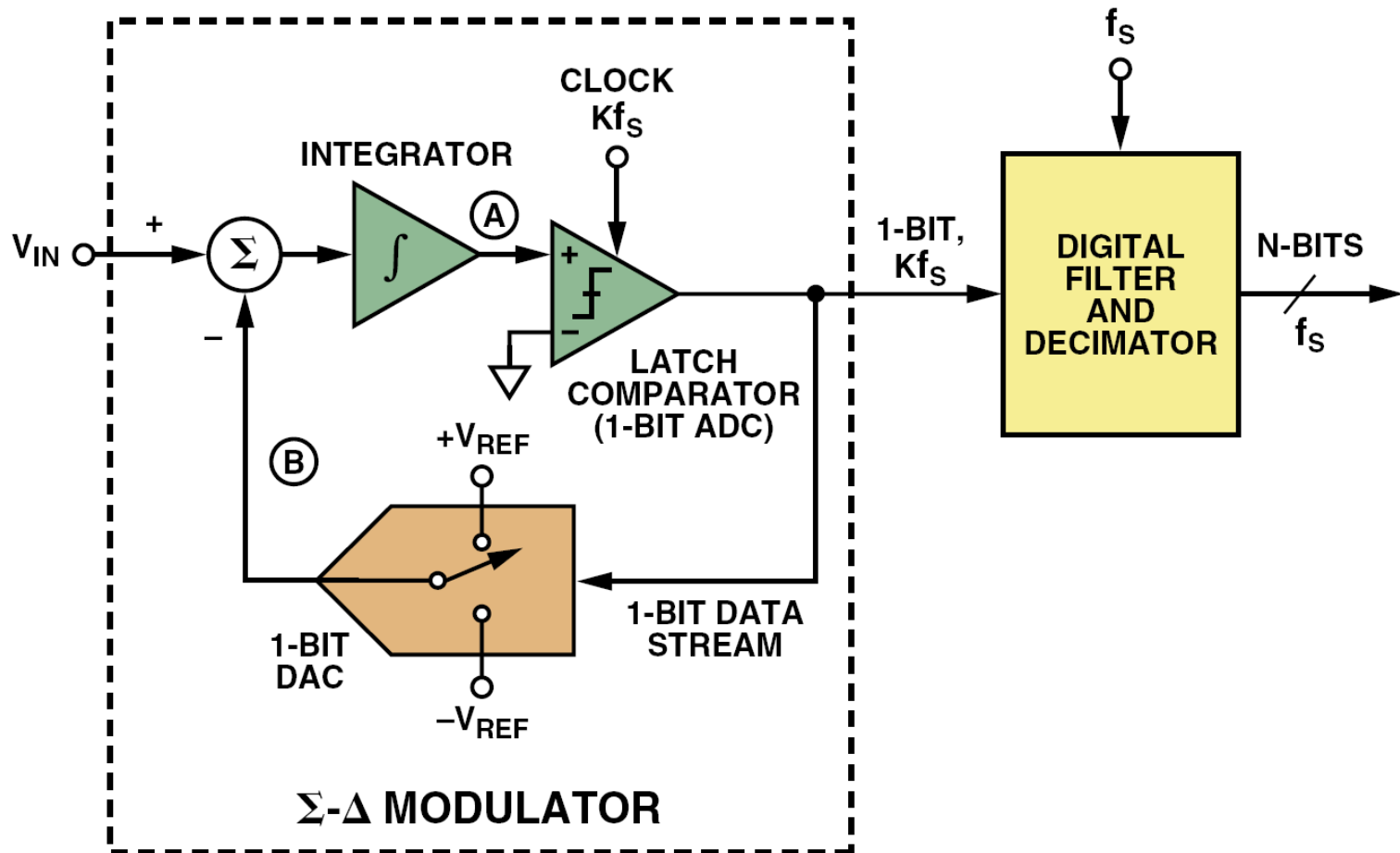

# Oversampling

- Sigma-delta converters use a technique called *oversampling* in order to achieve high-resolution outputs
- Oversampling is the process of ...
  - Sampling a signal with a sampling frequency significantly higher than twice the bandwidth or highest frequency of the signal being sampled.
- Oversampling
  - Reduces the sampling rate of the converter
  - And increases the ADC's resolution

# Sigma-Delta ADC

- Sigma-delta converters are ...
  - Low cost
  - High resolution
- And can be incorporated into many system-on-chip designs

# Pipelined ADCs ...

# Pipeline ADC

- The **pipeline** architecture is a variation on the flash ADC
- Therefore ...
  - A quick look at the Flash ADC ...


# Flash ADCs

- Sometimes called direct conversion or parallel ADCs
- Uses comparators for each decoded voltage range
- The comparator bank feeds a logic circuit that generates a code for each voltage range

# Flash ADCs

- Flash ADCs are the fastest converters on the market ...
  - ... but typically achieve only eight bits of resolution or less
- An 8-bit flash ADC would need 255 comparators in the circuit
  - This requires a large and expensive circuit
- Flash ADCs have a large die size ...
  - This in turn makes for high power consumption
- Flash ADCs are not the most accurate devices

# 3-bit Flash Converter

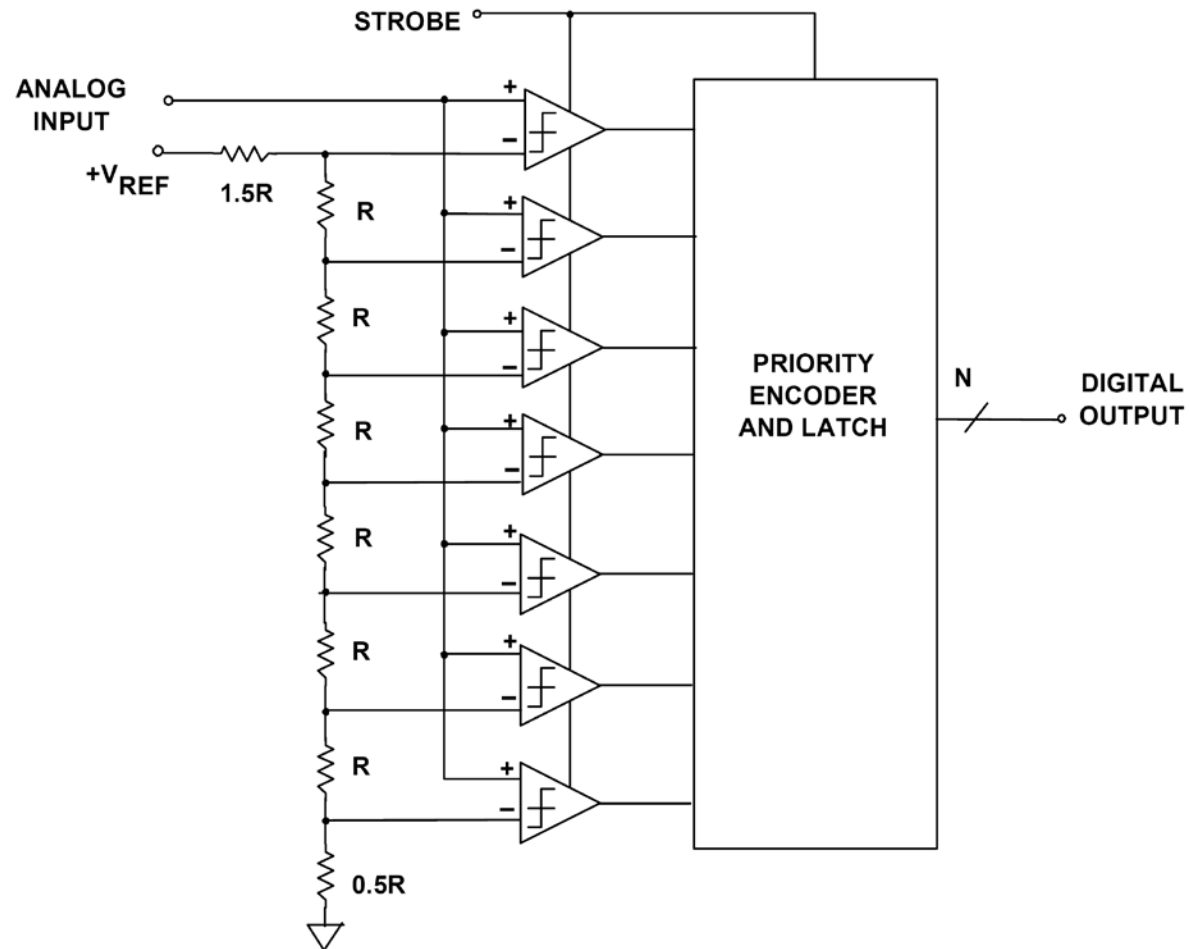



# Pipeline ADC

- A pipelined ADC separates the process into several different processes that can be performed in a successive order
- Basically, three processes take place within the device ...
  - There is a sample-and-hold circuit
  - A flash ADC
  - And a digital-to-analog converter


# How the Pipeline process works

- The sample-and-hold circuit samples the analog input signal
- The flash converter converts the sample to a digital value
- The digital value becomes the most significant bits of the eventual digital output
- This digital value is then fed into a similar resolution digital-to-analog converter, and ...
  - ... The analog output signal is subtracted from the original analog signal
- The difference of the two analog signals is then ...
  - Amplified and inputted into the next stage of the pipeline to have the same process repeated as in the first stage
- This process continues until the desired resolution is obtained

# Pipeline

- The resolution of the flash ADC and the DAC depend on the resolution of the pipelined ADC as a whole
- The pipelined ADC architecture is an alternative to the large size, power hungry flash ADC
- The pipeline ADC can offer ...
  - High resolution
  - And fast sampling rates
- But not as fast as the flash ADC


# Pipeline ADC

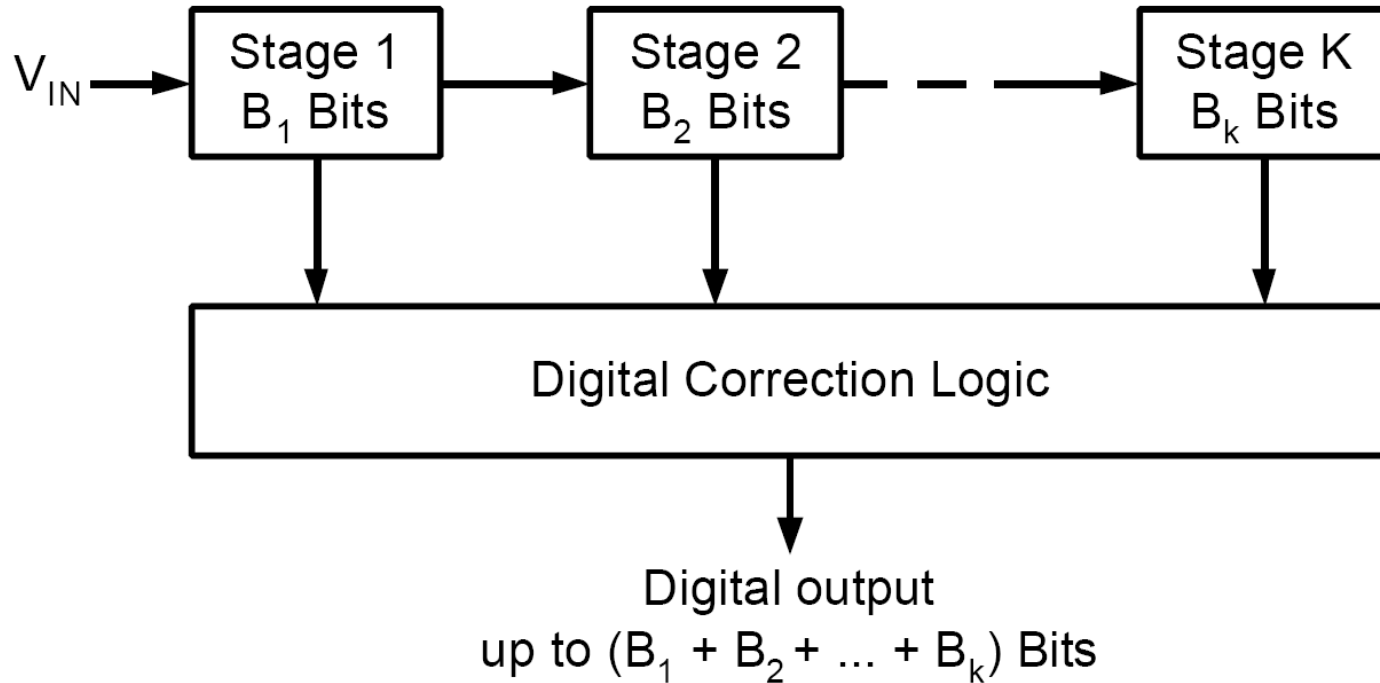

# ADCs Digital Output ...
 
# ADC Output

- LEDs (Digital) representation of Analog voltage ...




$$(\text{###h}) * (V_{\text{max}}/2^N) = \text{voltage}$$

$$2D5h = 725_{10}$$

$$(2D5h) * (5/2^{10}) = 3.54 \text{ volts}$$
 
# ADC Output – Minus bits 0 and 1

- LEDs (Digital) representation of Analog voltage ...



$$(\text{###h}) * (V_{\text{max}}/2^N) = \text{voltage}$$

$$2D4h = 724_{10}$$

$$2D7h = 727_{10}$$


~~$$(2D5h) * (5/2^{10}) = 3.54 \text{ volts}$$~~

$$(2D4h) * (5/2^{10}) = 3.53 \text{ volts}$$

$$(2D7h) * (5/2^{10}) = 3.55 \text{ volts}$$
 
# ADC Output – another method

- LEDs (Digital) representation of Analog voltage ...



$$(0bxxx) * (V_{max}/2^N) = \text{voltage}$$

$$(725_{10}) * (5/2^{10}) = 3.54 \text{ volts}$$

$(2^0) * 1 = 1$	$(2^5) * 0 = 0$
$(2^1) * 0 = 0$	$(2^6) * 1 = 64$
$(2^2) * 1 = 4$	$(2^7) * 1 = 128$
$(2^3) * 0 = 0$	$(2^8) * 0 = 0$
$(2^4) * 1 = 16$	$(2^9) * 1 = \underline{512}$
	<b>725</b>



# Table 1 – ADC804 Datasheet

TABLE 1. DECODING THE DIGITAL OUTPUT LEDs

HEX	BINARY	FRACTIONAL BINARY VALUE FOR		OUTPUT VOLTAGE CENTER VALUES WITH $V_{REF}/2=2.560 V_{DC}$	
		MS GROUP	LS GROUP	VMS GROUP (Note 15)	VLS GROUP (Note 15)
F	1 1 1 1	15/16	15/256	4.800	0.300
E	1 1 1 0	7/8	7/128	4.480	0.280
D	1 1 0 1	13/16	13/256	4.160	0.260
C	1 1 0 0	3/4	3/64	3.840	0.240
B	1 0 1 1	11/16	11/256	3.520	0.220
A	1 0 1 0	5/8	5/128	3.200	0.200
9	1 0 0 1	9/16	9/256	2.880	0.180
8	1 0 0 0	1/2	1/32	2.560	0.160
7	0 1 1 1	7/16	7/256	2.240	0.140
6	0 1 1 0	3/8	3/128	1.920	0.120
5	0 1 0 1	5/16	2/256	1.600	0.100
4	0 1 0 0	1/4	1/64	1.280	0.080
3	0 0 1 1	3/16	3/256	0.960	0.060
2	0 0 1 0	1/8	1/128	0.640	0.040
1	0 0 0 1	1/16	1/256	0.320	0.020
0	0 0 0 0			0	0

**Note 15:** Display Output=VMS Group + VLS Group

# Lab

# Lab #3 ...

## Lab #3– Overview

- To construct and operate an A/D Converter using the ADC804

# Next Class

# Next Class Topics

- Start/Finish Lab #3

# Homework

# Homework

1. Lab Reports – Lab report #2 is due 10/17/13
2. Read the following ...
  - The text ...
    - Pages 175 – 224 ... on-line Section 3.2, pages 3.39 – 3.103
    - Pages 231 – 248 ... on-line Section 3.3, pages 3.109 – 3.133
  - “Understanding analog to digital converter specifications”, by Len Stellar. Embedded Systems Design, 02/24/05
  - Which ADC Architecture is Right for Your Application, by Walt Kester. Analog Dialogue 39-06, June 2005
  - Freescale Semiconductor Application Note AN2438/D 2/2003

**The above articles can be found on the class web page**



**Time to start  
the lab ...**

# Lab

- Finish Lab #2 ... Start Lab #3

# Questions?

# References ...

# References

1. See within